

# Electronic Devices and Circuits

Jimmie J. Cathey

November 19, 2025

## 1 Circuit Analysis

### 1.1 Spice Elements

The passive and active circuit elements introduced in the previous section are all available in SPICE modeling; however, the manner of node specification and the voltage and current sense or direction are clarified for each element by Figure 1.1. The universal ground node is assigned the number 0. Otherwise, the node numbers  $n_1$  (positive node) and  $n_2$  (negative node) are positive integers selected to uniquely define each node in the network. The assumed direction of positive current flow is from the node  $n_1$  to node  $n_2$ . The four controlled sources—voltage-controlled voltage source (VCVS), current-controlled voltage source (CCVS), voltage-controlled current source (VCCS), and current-controlled current source (CCCS)—have the associated controlling element also shown with its nodes indicated by  $cn_1$  (positive) and  $cn_2$  (negative). Each element is described by an *element specification statement* in the SPICE netlist code. Table 1.1 presents the basic format for the element specification statement for each of the elements in Figure 1.1. The first letter of the element name specifies the device and the remaining characters must assure a unique name.

### 1.2 Network Theorems

**Example 1.1.** Use SPICE methods to determine the Thévenin equivalent circuit looking to the left through terminals 3,0 for the circuit of Figure 1.1. In SPICE independent source models, an ideal voltage source of 0V acts as a short circuit and an ideal current source of 0 A acts as an infinite impedance

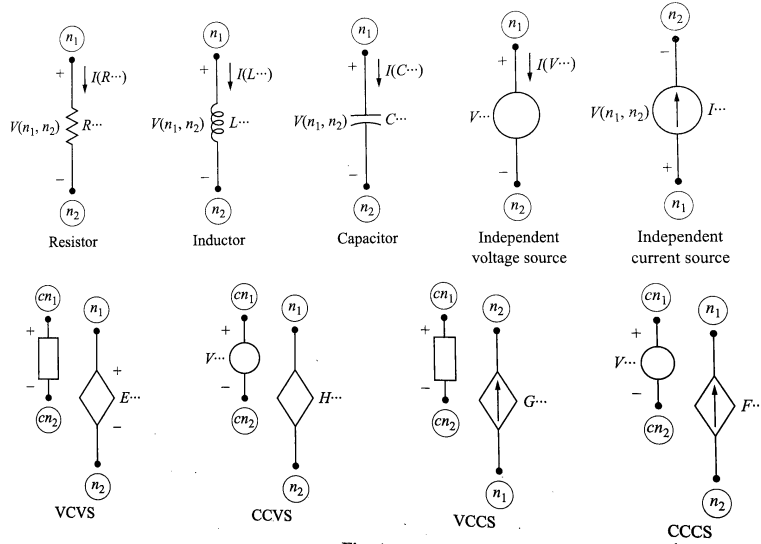


Fig. 1-2

Element	Name	Signal Type	Control Source	Value
Resistor	R...			$\Omega$
Inductor	L...			H
Capacitor	C...			F
Voltage source	V...	AC or DC <sup>a</sup>		V <sup>b</sup>
Current source	I...	AC or DC <sup>a</sup>		A <sup>b</sup>
VCVS	E...		(cn1, cn2)	V/V
CCVS	H...		V...	V/A
VCCS	G...		(cn1, cn2)	A/V
CCCS	F...		V...	A/A

a. Time-varying signal types (SIN, PULSE, EXP, PWL, SFFM) also available.

b. AC signal types may specify phase angle as well as magnitude.

or open circuit. Advantage will be taken of these two features to solve the problem.

Load resistor  $R_L$  of Figure 1.1(a) is replaced by the driving point current source  $I_{dp}$  of Figure 1.1(b). The netlist code that follows forms a SPICE description of the resulting circuit. The code is set up with parameter-assigned values for  $V_1$ ,  $I_2$ , and  $I_{dp}$ .

```
Ex1_5.CIR - Thevenin equivalent circuit
.PARAM V1value=0V I2value=0A Idpvalue=1A
```

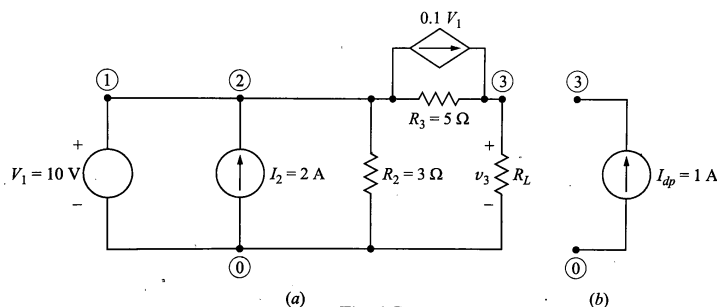


Fig. 1-7

```

V1 1 0 DC {V1value}
R1 1 2 1ohm
I2 0 2 DC {I2value}
R2 2 0 3ohm
R3 2 3 5ohm
G3 2 3 (1,0) 0.1 ; Voltage-controlled current-source
Idp 0 3 DC {Idpvalue}
.END

```

If both  $V_1$  and  $I_2$  are deactivated by setting  $V1value=I2value=0$ , current  $I_{dp} = 1$  A must flow through the Thévening equivalent impedance  $Z_{Th} = R_{Th}$  so that  $v_3 = I_{dp} R_{Th} = R_{Th}$ . Execution of `<Ex1_5.CIR>` by a SPICE program writes the values of the node voltages for nodes 1, 2, and 3 with respect to the universal ground node 0 in a file `<Ex1_5.OUT>`. Poll the output file to find  $v_3 = V(3) = R_{Th} = 5.75 \Omega$ .

In order to determine  $V_{Th}$  (open-circuit voltage between terminals 3,0), edit `<Ex1_5.CIR>` to set  $V1value=10V$ ,  $I2value=2A$ , and  $Idpvalue=0A$ . Execute `<Ex1_5.CIR>` and poll the output file to find  $V_{Th} = v_3 = V(3) = 14$  V.

### 1.3 Two-Port Networks

The  $z$  parameters and the  $H$  parameters can be numerically evaluated by SPICE methods. In electronics applications, the  $z$  and  $h$  parameters find application in analysis when small ac signals are impressed on circuits that exhibit limited-range linearity. Thus, in general, the test sources in the SPICE analysis should be of magnitudes comparable to the impressed signals of the anticipated application. Typically, the devices used in an electronic circuit will have one or more dc sources connected to bias or that place the device at a favorable point of operation. The input and output ports may be coupled by large capacitors that act to block the appearance of any dc

voltages at the input and output ports while presenting negligible impedance to ac signals. Further, electronic circuits are usually frequency-sensitive so that any set of  $z$  or  $h$  parameters is valid for a particular frequency. Any SPICE-based evaluation of the  $z$  and  $h$  parameters should be capable of addressing the above outlined characteristics of electronics circuits.

## 2 Semiconductor Diodes

### 2.1 The Ideal Diode

 


Fig. 2-1

### 2.2 Diode Terminal Characteristics

Use of the Fermi-Dirac probability function to predict charge neutralization give the *static* (non-time-varying) equation for diode junction current:

$$i_D = I_0(e^{v_D/\eta V_T} - 1) A \quad (1)$$

where

$$V_T \equiv kT/q, \text{ V}$$

$$v_D \equiv \text{diode terminal voltage, V}$$

$$I_0 \equiv \text{temperature-dependent saturation current, A}$$

$$T \equiv \text{absolute temperature of } p\text{-}n \text{ junction, K}$$

$$k \equiv \text{Boltzmann's constant } (1.38 \times 10^{-23} \text{ J/K})$$

$$q \equiv \text{electron charge } (1.6 \times 10^{-19} \text{ C})$$

$$\eta \equiv \text{empirical constant, 1 for Ge and 2 for Si}$$

## 2.3 The Diode SPICE Model

The element specification statement for a diode must explicitly name a model even if the default model parameters are intended for use. The general form of the diode specification statement is as follows, where the *model name* is arbitrarily chosen:

$$D \cdots n_1 n_2 \text{ model name}$$

Node  $n_1$  is the anode and node  $n_2$  is the cathode of the diode. Positive current and voltage directions are clarified by Figure 2.1(b).

In addition, the .MODEL control statement must be added to the netlist code even if the default parameters are acceptable. This control statement is

$$\text{MODEL model name D (parameters)}$$

If the parameters field is left blank, default values are assigned. Otherwise, the parameters field contains the number of desired specifications in the format *parameter name = value*. Specific parameters of concern in this book are documented by Table 2.3.

Parameter	Description	Reference	Default	Units
Is	saturation current	$I_0$ of (1)	$1 \times 10^{-14}$	A
n	emission coefficient	$\eta$ of (1)	1	
BV	reverse breakdown voltage	$V_R$ of Figure ??	$\infty$	V
IBV	reverse breakdown current	$I_R$ of Figure ??	$1 \times 10^{-10}$	A
Rs	ohmic resistance	Subsection 2.2)	0	$\Omega$

## 3 Characteristics of Bipolar Junction Transistors

### 3.1 BJT SPICE Model

The element specification statement for a BJT must explicitly name a model even if the default model parameters are intended for use. The general form of the transistor specification statement is as follows:

$$Q \cdots n_1 n_2 n_3 \text{ model name}$$

Nodes  $n_1$ ,  $n_2$ , and  $n_3$  belong to the collector, base, and emitter, respectively. The *model name* is an arbitrary selection of alpha and numeric characters to uniquely identify the model. Positive current and voltage directions for the *pn*p and *np*n transistor are clarified by Figure ??.

In addition, a .MODEL control statement must be added to the netlist code. This control statement specifies whether the transistor is *pn*p or *np*n and thus has one of the following two forms:

MODEL *model name* PNP (*parameters*)  
 MODEL *model name* NPN (*parameters*)


If the parameter field is left blank, default values are assigned. Non-default desired parameter specifications are entered in the parameter field using the format *parameter name* = *value*. Specific parameters that are of concern in this book are documented in Table 3.1.

All parameter values are entered with positive values regardless of whether the transistor is *pn*p or *np*n. Two transistor models will be used in this chapter—*generic model* and *default model*—as introduced in

Parameter	Description	Major Impact	Default	Units
Is	saturation current	$\uparrow I_s, \downarrow V_{BEQ}$	$1 \times 10^{-16}$	A
Ikf	high current roll-off	$\downarrow I_{kf}, \downarrow I_C$	$\infty$	A
Isc	base-collector leakage	$\uparrow I_{sc}, \uparrow I_C$	0	A
Bf	forward current gain	$\uparrow B_f, \uparrow I_C$	100	
Br	reverse current gain	$\uparrow B_r, \uparrow \text{rev. } I_C$	1	
Rb	base resistance	$\uparrow R_b, \downarrow di_B/dv_{BE}$	0	$\Omega$
Rc	collector resistance	$\uparrow R_c, \uparrow V_{CEsat}$	0	$\Omega$
Va	forward Early voltage	$\uparrow V_a, \uparrow di_C/dt$	$\infty$	V
Cjc	base-collector capacitance	high freq. response	0	F
Cje	base-emitter capacitance	high freq. response	0	F

**Example 3.1.** Use SPICE methods to generate the CE collector characteristics for an *np*n transistor characterized by (a) the default parameter values and (b) a reasonable set of values for the parameters appearing in Table 3.1.

```
Ex3_2.CIR
Ib 0 1 0uA
Q 2 1 0 QNPN
*Q 2 1 0 QNPNG
VC 2 0 0V
```

 

**Fig. 3-5**

```
.MODEL QNPN NPN() ; Default BJT
*.MODEL QNPNG NPN(Is=10fA Ikf=150mA Isc=10fA Bf=150
** Br=3 Rb=1ohm Rc=1ohm Va=30V Cjc=10pF Cje=15pf)
.DC VC 0V 15V 1V Ib 0uA 150uA 25uA
.PROBE
.END
```

## 4 Characteristics of Field-Effect Transistors and Triodes

### 4.1 JFET SPICE Model

The element specification statement for a JFET must explicitly assign a *model name* that is an arbitrary selection of alpha and numeric characters.

Parameter	Description	Major Impact	Default	Units
Vto	pinchoff voltage	shorted-gate current	-2	V
Beta	transcond. coeff.	shorted-gate current	0.0001	A/V <sup>2</sup>
Rd	drain resistance	current limit	0	$\Omega$
Rs	source resistance	current limit	0	$\Omega$
CGS	gate-source cap.	high frequency	0	F
CGD	gate-drain cap.	high frequency	0	F

### 4.2 MOSFET SPICE Model

Parameter	Description	Default	Units
Vto	Threshold voltage	0	V
Kp	Transcond. coeff.	$2 \times 10^{-5}$	A/V <sup>2</sup>
Rd	Drain resistance	0	$\Omega$
Rg	Gate resistance	0	$\Omega$